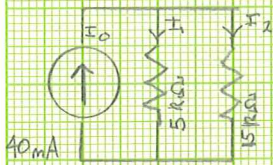


$V_0 = 120V$
 $V_{23} = 100V$
 $V_i = V_0 \frac{R_i}{R_{eq}}$


$100 = 120 \cdot \frac{1.4}{1.4 + R_{L1}} \rightarrow R_{L1} = 0.28 \Omega$

VOLTAGE DIVIDER




$I_i = I_0 \frac{R_{eq}}{R_i}$
 $I_1 = 40mA \frac{3750}{5000} = 30mA$
 $I_2 = 40mA \frac{3750}{5000} = 10mA$

CURRENT DIVIDER

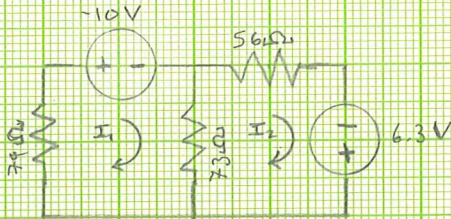


$I_1: 79 \Omega I_1 + 10V + 73 \Omega (I_1 - I_2) = 0$
 $I_2: 73 \Omega (I_1 - I_2) + 56 \Omega I_2 - 6.3V = 0$
 rref $\begin{bmatrix} 79+73 & -73 & 10 \\ -73 & 73+56 & 6.3 \end{bmatrix} \rightarrow I_1 = 0.123A$
 $I_2 = 0.118A$

MESH CURRENT

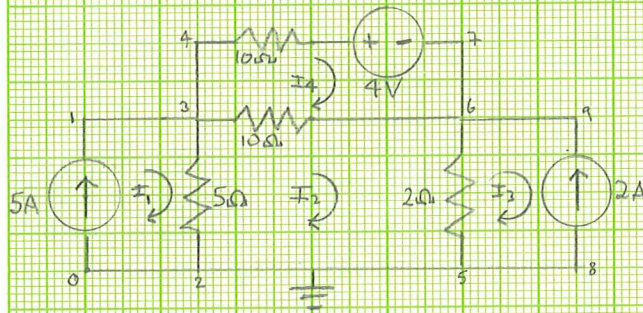


$I_1: -V_{01} + 5 \Omega (I_1 - I_2) = 0$
 $I_2: 5 \Omega (I_1 - I_2) + 10 \Omega (I_2 - I_4) + 2 \Omega (I_2 - I_3) = 0$
 $-5 \Omega I_1 + 17 \Omega I_2 - 2 \Omega I_3 - 10 \Omega I_4 = 0$
 $I_3: 2 \Omega (I_3 - I_2) + V_{03} = 0$
 $I_4: 10 \Omega I_4 + 4V + 10 \Omega (I_4 - I_2) = 0$
 $-10 \Omega I_2 + 20 \Omega I_4 = -4V$
 $I_1 = 5A \quad I_3 = -2A \quad I_4 = \frac{-4 + 10 I_2}{20} = 0.59A$
 $I_2 = 1.58A$

NODE VOLTAGE

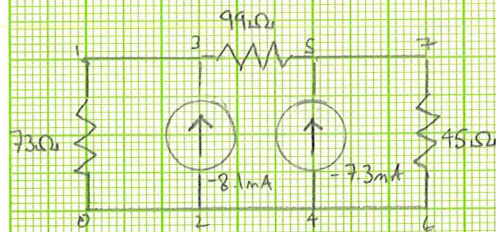

$V_3: I_{3\uparrow} = -8.1mA \quad I_{3\downarrow} = \frac{V_3 - 0}{99 \Omega} \quad I_{3\rightarrow} = \frac{V_3 - V_5}{99 \Omega} \quad \sum I_i = 0$
 $V_5: I_{5\uparrow} = -7.3mA \quad I_{5\downarrow} = \frac{V_5 - V_3}{99 \Omega} \quad I_{5\rightarrow} = \frac{V_5 - 0}{45 \Omega} \quad \sum I_i = 0$
 $V_2 (\frac{1}{99} + \frac{1}{99}) + V_5 (-\frac{1}{99}) = 8.1mA$
 $V_2 (-\frac{1}{99}) + V_5 (\frac{1}{99} + \frac{1}{45}) = 7.3mA$
 rref $\begin{bmatrix} \frac{1}{73} + \frac{1}{99} & -\frac{1}{99} & 8.1 \times 10^{-3} \\ -\frac{1}{99} & \frac{1}{99} + \frac{1}{45} & 7.3 \times 10^{-3} \end{bmatrix} \rightarrow V_2 = 0.503V$
 $V_5 = 0.383V$

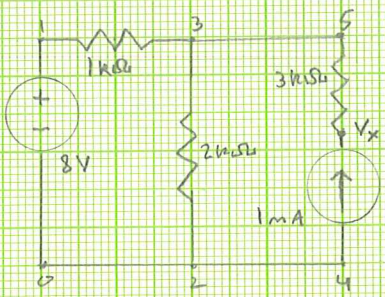

NODE VOLTAGE


$$V_3: I_{3L} = \frac{V_3 - 8}{1000} \quad I_{3D} = \frac{V_3 - 0}{2000} \quad I_{3R} = \frac{V_3 - V_x}{3000} \quad \sum I_3 = 0$$

$$V_x: I_{xL} = \frac{V_x - V_3}{2000} \quad I_{xR} = -1 \times 10^{-3} \quad \sum I_x = 0$$


$$V_3 \left(\frac{1}{1000} + \frac{1}{2000} + \frac{1}{3000} \right) + V_x \left(-\frac{1}{2000} \right) = \frac{8}{1000}$$

$$V_3 \left(-\frac{1}{3000} \right) + V_x \left(\frac{1}{3000} \right) = 1 \times 10^{-3}$$
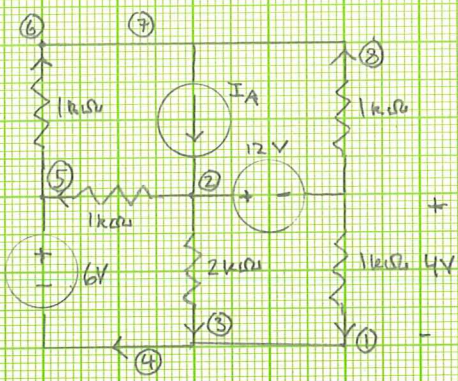
$$r_{ref} \begin{bmatrix} \frac{1}{1000} + \frac{1}{2000} + \frac{1}{3000} & -\frac{1}{3000} \\ -\frac{1}{3000} & \frac{1}{3000} \end{bmatrix} \begin{bmatrix} V_3 \\ V_x \end{bmatrix} = \begin{bmatrix} \frac{8}{1000} \\ 1 \times 10^{-3} \end{bmatrix} \rightarrow \begin{bmatrix} V_3 = 6V \\ V_x = 9V \end{bmatrix}$$



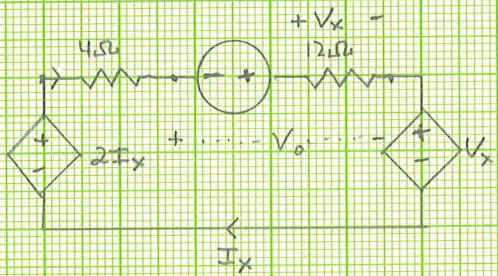- CIRCUIT ANALYSIS**
- $\frac{4V}{1000\Omega} = 4mA$
 - $4V + 12V = 16V$
 - $\frac{16V}{2000\Omega} = 8mA$
 - $4mA + 8mA = 12mA$
 - $\frac{16V - 6V}{1000\Omega} = 10mA$
 - $12mA + 10mA = 22mA$
 - $6V - 22mA \cdot 1000\Omega = -16V$
 - $\frac{4V - 16V}{1000\Omega} = -12mA$
- $I_A = 22mA + 20mA = 42mA$




DEPENDENT SOURCE

$$-2I_x + 4I_x - 12 - V_x + V_x = 0 \rightarrow I_x = 6$$


$$V_x = 6A \cdot 12\Omega = 72V$$

$$V_o = -12 - 72 = 60V$$

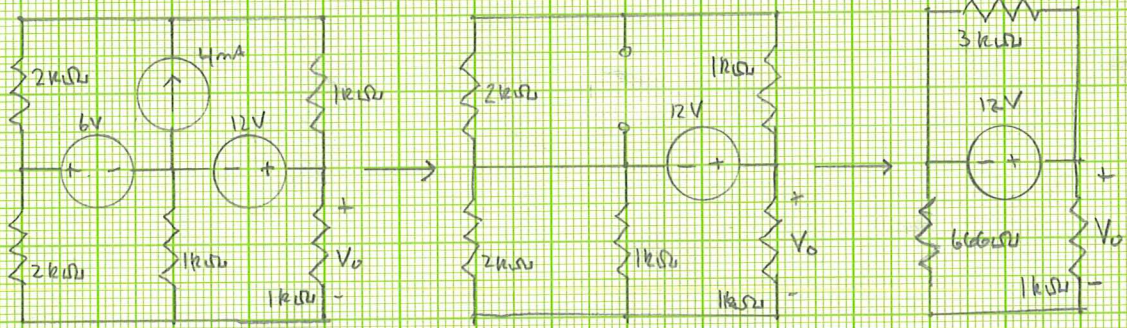


SUPERPOSITION

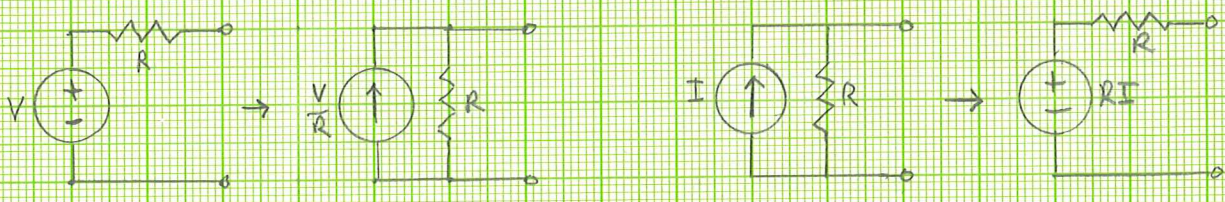FIND PORTION OF V_o FROM 12V SOURCE: $V_o = \frac{1000}{1000 + 6000} \cdot 12V = 7.2V$



SOURCE TRANSFORMATION

Ex 1

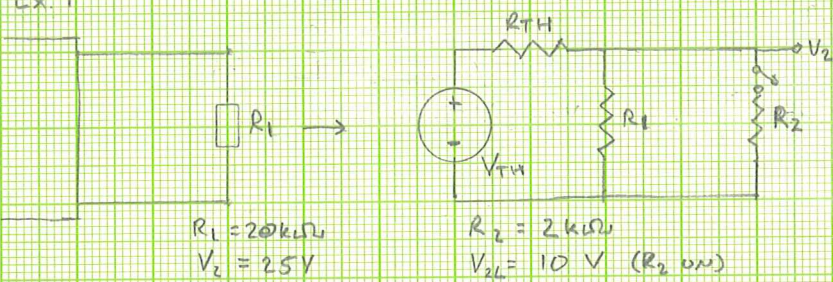

$R_1 = 20k\Omega$
 $V_2 = 25V$

$R_2 = 2k\Omega$
 $V_{2L} = 10V (R_2 \text{ on})$


THEVENIN

Let $d = [R_1 \cdot V_{2L} + R_2 (V_{2L} - V_2)]^{-1}$

$V_{TH} = V_2 \cdot V_{2L} \cdot R_1 \cdot d = 29.4V$

$R_{TH} = R_1 \cdot R_2 \cdot (V_2 - V_{2L}) \cdot d = 3529\Omega$




Ex 2

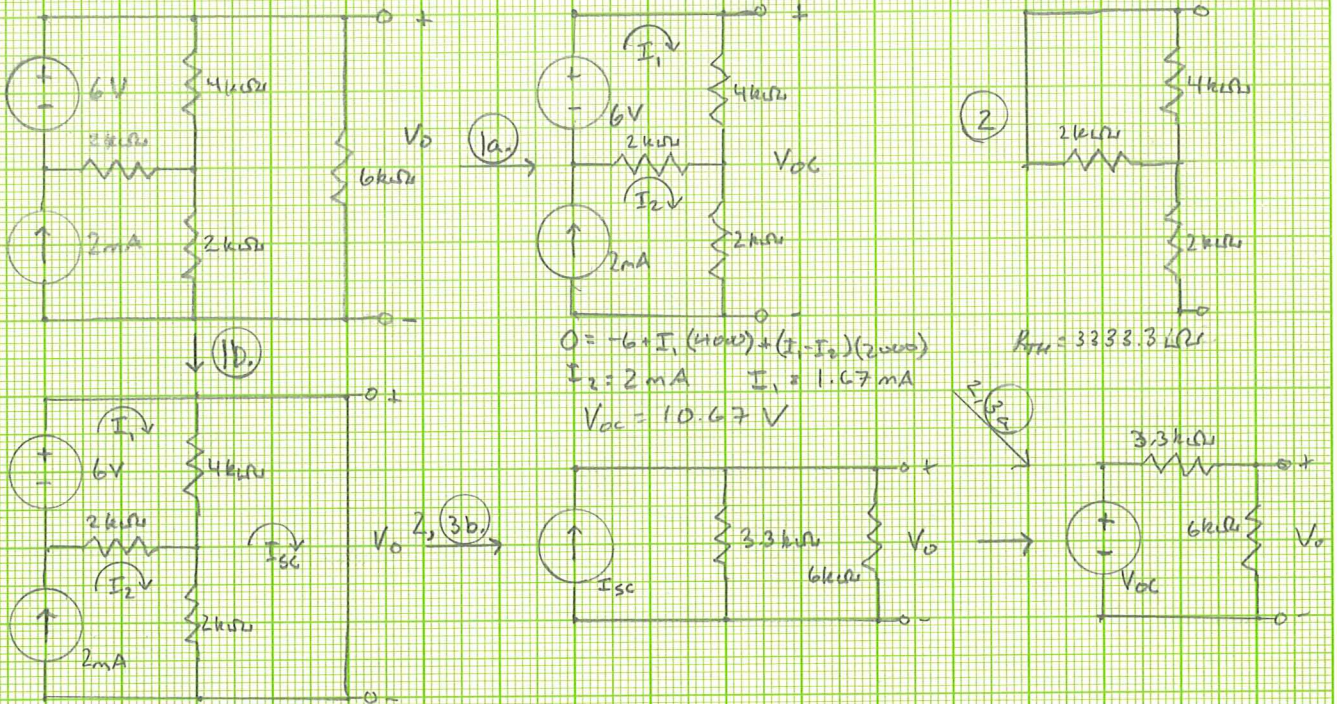

$0 = -6 + I_1(4000) + (I_1 - I_2)(2000)$
 $I_2 = 2mA \quad I_1 = 1.67mA$
 $V_{oc} = 10.67V$

$R_{TH} = 3333.3\Omega$

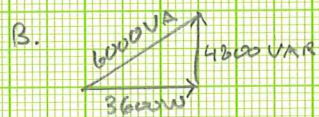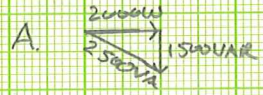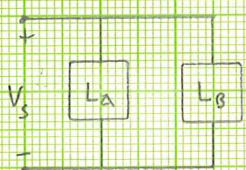
$0 = -6 + (I_1 - I_{sc})(4000) + (I_1 - I_2)(2000)$
 $0 = -(I_1 - I_{sc})(4000) - (I_2 - I_{sc})(2000)$
 $I_1 = 3.8mA \quad I_{sc} = 3.2mA$




POWER

LOAD A: 2kW, p.f. = 0.8 LEADING $|S| = \frac{P}{p.f.} \rightarrow S = 2500VA$
LOAD B: 6kVA, p.f. = 0.6 LAGGING $P = |S| \cdot p.f. \rightarrow P = 3600W$


ST: DON'T SUM S_i ; ADD VECTORS

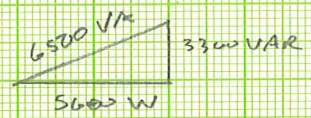


LEADING

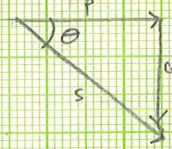


LAGGING

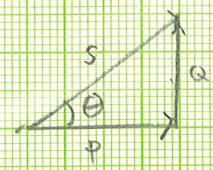

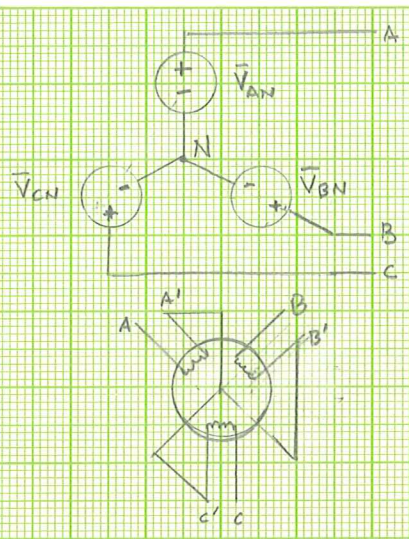

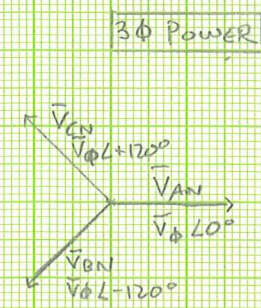
$$\begin{aligned} \vec{V}_{AB} &= \vec{V}_{AN} - \vec{V}_{BN} = \vec{V}_{AN} \sqrt{3} \angle 30^\circ \\ \vec{V}_{BC} &= \vec{V}_{BN} - \vec{V}_{CN} = \vec{V}_{BN} \sqrt{3} \angle 30^\circ \\ \vec{V}_{CA} &= \vec{V}_{CN} - \vec{V}_{AN} = \vec{V}_{CN} \sqrt{3} \angle 30^\circ \\ \vec{V}_{AN} + \vec{V}_{BN} + \vec{V}_{CN} &= 0 \quad \vec{V}_L = \vec{V}_\phi \sqrt{3} \angle 30^\circ \end{aligned}$$




3φ POWER

Y-Y


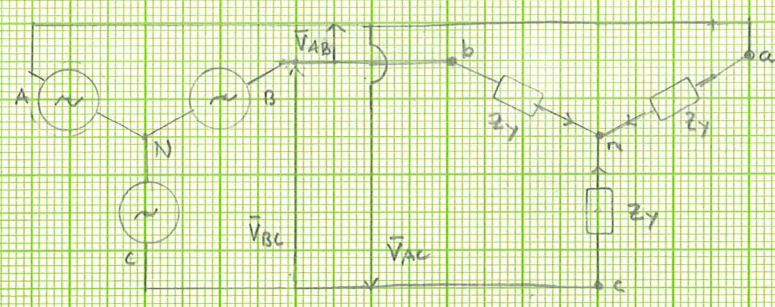


$$\begin{aligned} \vec{I}_{An} &= \frac{\vec{V}_{AN}}{Z_Y} \quad \vec{I}_{Bn} = \frac{\vec{V}_{BN}}{Z_Y} \quad \vec{I}_{Cn} = \frac{\vec{V}_{CN}}{Z_Y} \quad \Delta\phi = 120^\circ \\ S_{\phi a} &= \vec{V}_{AN} \vec{I}_{An}^* \quad S_T = 3S_{\phi} \\ \vec{V}_{AB} &= \vec{V}_\phi \sqrt{3} \angle 30^\circ \quad \vec{V}_\phi = \vec{V}_{AN} \end{aligned}$$

Δ-Δ

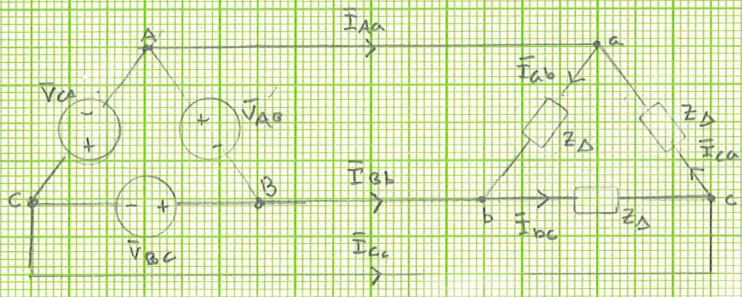

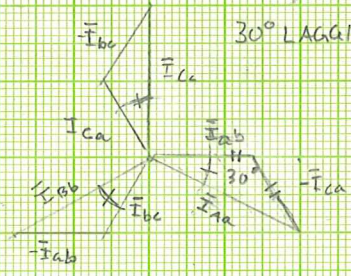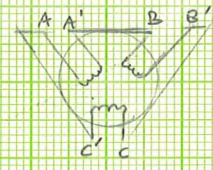
$$\begin{aligned} \vec{I}_{ab} &= \frac{\vec{V}_{AB}}{Z_\Delta} \quad \vec{I}_{bc} = \frac{\vec{V}_{BC}}{Z_\Delta} \quad \vec{I}_{ca} = \frac{\vec{V}_{CA}}{Z_\Delta} \quad \Delta\phi = 120^\circ \\ S_{\phi a} &= \vec{V}_{AB} \vec{I}_{ab}^* \quad S_T = 3S_{\phi} \\ \vec{V}_{ab} &= \vec{V}_{AB} \end{aligned}$$




30° LAGGING
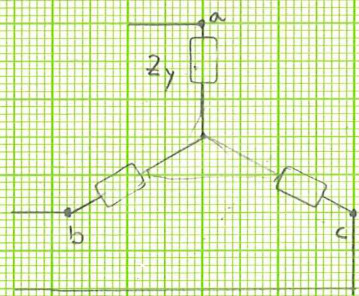
$$\begin{aligned} \vec{I}_{Aa} &= \vec{I}_{ab} - \vec{I}_{ca} = \vec{I}_{ab} \sqrt{3} \angle 30^\circ \\ \vec{I}_{Bb} &= \vec{I}_{bc} - \vec{I}_{ab} = \vec{I}_{bc} \sqrt{3} \angle 30^\circ \\ \vec{I}_{Cc} &= \vec{I}_{ca} - \vec{I}_{bc} = \vec{I}_{ca} \sqrt{3} \angle 30^\circ \end{aligned}$$




$$\begin{aligned} S_{\phi a} &= \vec{V}_{an} \vec{I}_{an}^* \\ S_T &= 3S_{\phi} \\ S_T &= 3|\vec{V}_{an}| |\vec{I}_{an}| \angle \phi_2 \\ S_T &= 3 \left| \frac{\vec{V}_L}{\sqrt{3}} \right| |\vec{I}_L| \angle \phi_2 \\ S_T &= \sqrt{3} |\vec{V}_L| |\vec{I}_L| \angle \phi_2 \\ \vec{I}_L &= \vec{I}_{an} = \vec{I}_{bn} = \vec{I}_{cn} \\ Z_Y &= \frac{Z_\Delta}{3} \end{aligned}$$

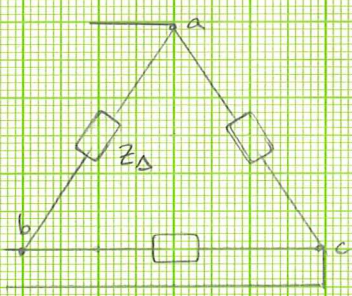


$$\begin{aligned} S_{\phi a} &= \vec{V}_{ab} \vec{I}_{ab}^* \\ S_T &= 3S_{\phi} \\ S_T &= 3|\vec{V}_{ab}| |\vec{I}_{ab}| \angle \phi_2 \\ S_T &= 3|\vec{V}_L| \left| \frac{\vec{I}_L}{\sqrt{3}} \right| \angle \phi_2 \\ S_T &= \sqrt{3} |\vec{V}_L| |\vec{I}_L| \angle \phi_2 \\ \vec{V}_L &= \vec{V}_{ab} = \vec{V}_{bc} = \vec{V}_{ca} \\ Z_\Delta &= 3Z_Y \end{aligned}$$



MUTUAL INDUCTANCE

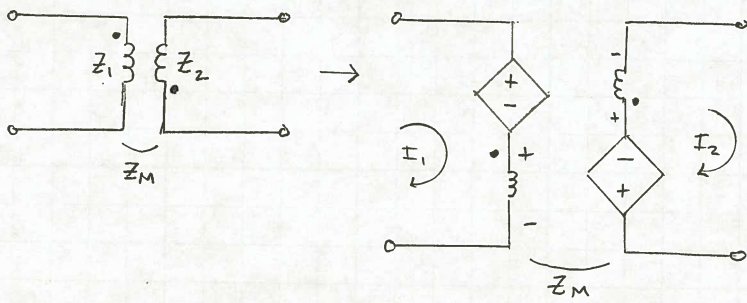

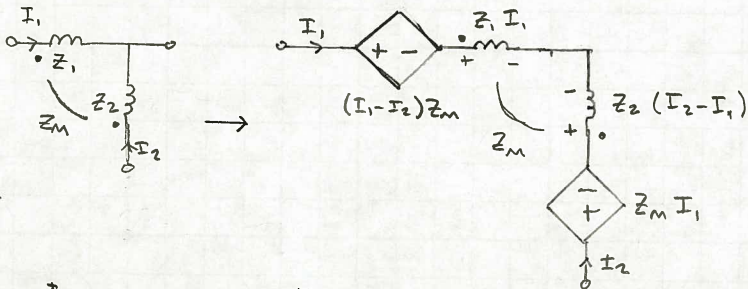
CURRENT INTO DOT PRODUCES POSITIVE
 CURRENT OUT OF THE OTHER
 CURRENT FLOWS THROUGH INDUCTOR
 IN DIRECTION OF DROP
 $\pm L_m I_1 I_2$ DEPENDING ON WHETHER
 CURRENTS IN/OUT OF DOTS
 HAVE SAME DIRECTION



IDEAL TRANSFORMER

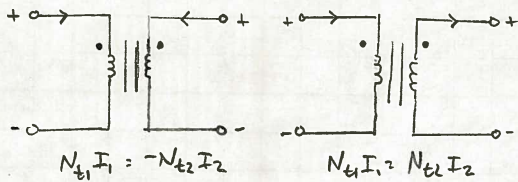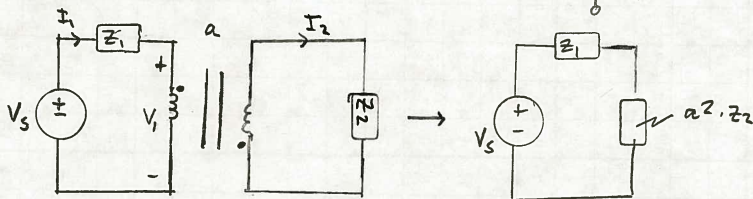

AMPAD

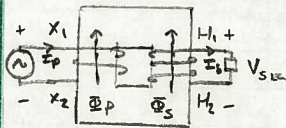


$$X_1(+)\rightarrow H_1(+)$$

CURRENT IN $X_1 \rightarrow$ CURRENT OUT H_1

CURRENT FLOWS IN
DIRECTION OF V DROP

1 ϕ TRANSFORMER

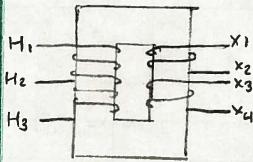


$$H_1-H_2 \quad 208V$$

$$H_1-H_2 \quad 104V$$

$$X_1-X_2 \quad 120V$$


$$X_3-X_4 \quad 120V$$

1 kVA

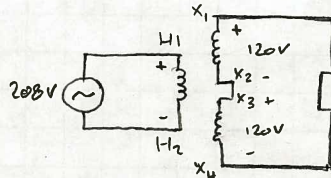

$$H_1(+)\rightarrow X_1(+), X_3(+)$$

208/240 V CONFIG.

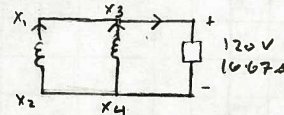


$$I_{RATED} = \frac{1 \text{ kVA}}{120V} = 8.33A$$

(COIL)

208/120V CONFIG.

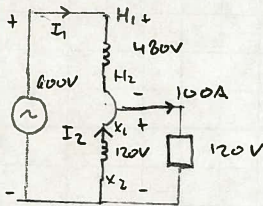480/120 V 60Hz 9.6 kVA \rightarrow 600/120V



$$I_1 \text{ RATED} = \frac{9600VA}{480V} = 20A$$

$$I_2 \text{ RATED} = \frac{9600VA}{120V} = 80A = 4I_1$$

CURRENT IN $H_1 \rightarrow$ CURRENT OUT X_1


$$S_T = 12 \text{ kVA}$$

V RATIO IS ALWAYS THE SAME. CURRENT CANNOT BE HIGHER.

AUTO TRANSFORMER

SERIESED COILS


480/600V

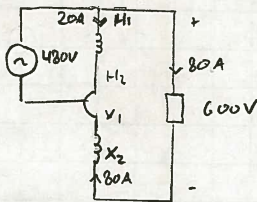

I_{1R}, I_{2R} DON'T CHANGE


$$S_T = 480 \text{ kVA}$$

300/120 V

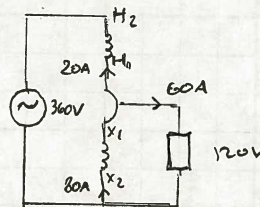

$$S_T = 7.2 \text{ kVA}$$

AMPAD™

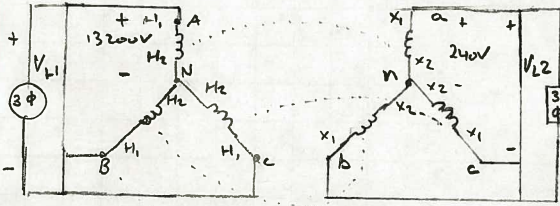

$$\bar{V}_{L1} = \sqrt{3} \bar{V}_{AN} = 22863 \text{ V}$$

$$\bar{V}_{L2} = \sqrt{3} \bar{V}_{an} = 415.7 \text{ V}$$

3 ϕ TRANSFORMER


$$\bar{I}_{AN} = \frac{59400}{13200} = 4.5 \text{ A}$$

$$\bar{I}_{na} = \frac{59400}{240} = 247.5 \text{ A}$$

IN $H_1 \rightarrow$ OUT OF X_1

3 x 13200/240V 60 Hz 59.4 kVA

$$S_T = \sqrt{3} |\bar{V}_L| |\bar{I}_L| = 178.2 \text{ kVA (SAME FOR 1 \& 2)}$$

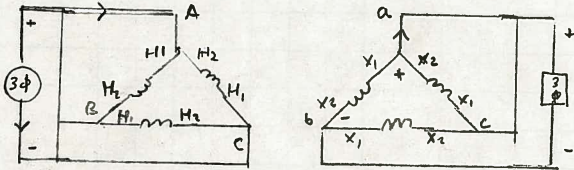


$$\bar{I}_{ab} = \frac{59400}{240} = 247.5 \text{ A} \quad \bar{I}_{L2} = \sqrt{3} \cdot 247.5 \text{ A} = 428.7 \text{ A}$$

$$\bar{I}_{AB} = \frac{59400}{13200} = 4.5 \text{ A} \quad \bar{I}_{L1} = \sqrt{3} \cdot 4.5 \text{ A} = 7.794 \text{ A}$$

$$\bar{V}_{ab} = 240 \text{ V} \quad \bar{V}_{AB} = 13200 \text{ V}$$

$$S_T = \sqrt{3} |\bar{V}_L| |\bar{I}_L| = 178.2 \text{ kVA}$$

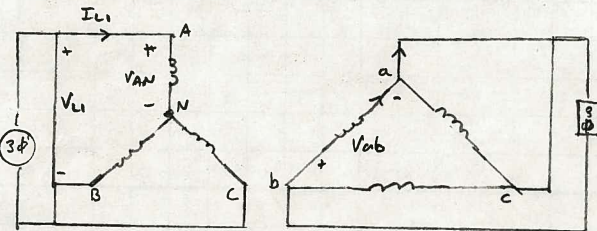


$$\bar{V}_{L1} = 13200 \text{ V} \quad \bar{V}_{AN} = \frac{13200}{\sqrt{3}} = 7621 \text{ V}$$

$$\bar{I}_{L1} = \frac{59400}{13200} = 4.5 \text{ A} \quad \bar{V}_{ab} = 240 \text{ V}$$

$$S_T = 3 (13200 \text{ V} \cdot 4.5 \text{ A}) = 178.2 \text{ kVA}$$

3 x 7621V/240V 60 Hz 59.4 kVA

$$a = 31.8$$

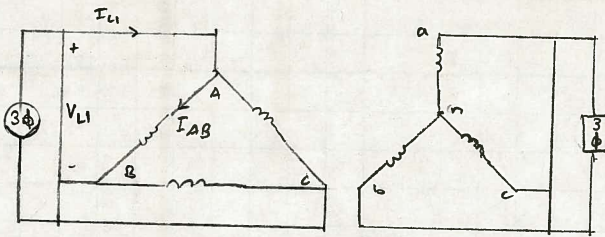

$$\bar{V}_{L1} = 13200 \text{ V} \quad \bar{V}_{AB} = 13200 \text{ V}$$


$$\bar{I}_{L1} = \frac{59400}{13200} = 4.5 \text{ A}$$

$$\bar{V}_{an} = \frac{V_L}{\sqrt{3}} = 138.6 \text{ V}$$

$$S_T = (13200 \text{ V} \cdot 4.5 \text{ A} \cdot 3) = 178.2 \text{ kVA}$$

3 x 13200V/138.6V 60 Hz 59.4 kVA

$$a = 95.2$$

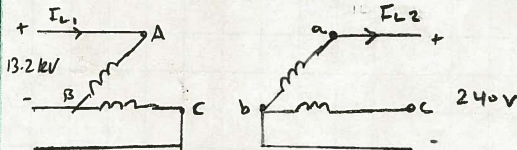


$$I_{L2} = \frac{59400}{\sqrt{3} \cdot 240} = 142.9 \text{ A}$$

$$I_{L1} = \frac{59400}{\sqrt{3} \cdot 13200} = 2.6 \text{ A}$$

$$S_T = I_{L1} \cdot V_{L1} = 34320 \text{ VA} \neq 25 \phi$$


2 x 13200V/240V 60 Hz 34320VA

AMPAD

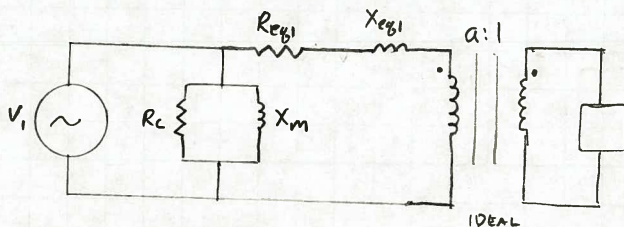


$$R_{eq1} = R_1 + a^2 R_2 \quad X_{eq1} = X_1 + a^2 X_2$$

REAL TRANSFORMER

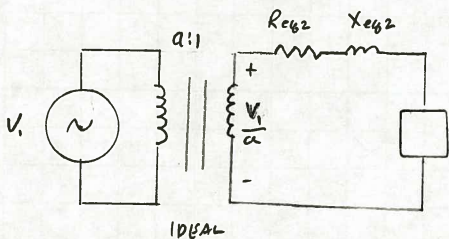

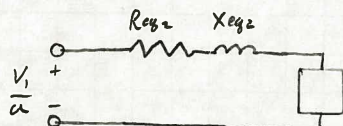
$$R_{eq2} = \frac{R_{eq1}}{a^2} \quad X_{eq2} = \frac{X_{eq1}}{a^2}$$



$$\frac{V_1}{a} = \sqrt{(V_L \cos \phi + I_L R_{eq2})^2 + (V_L \sin \phi \pm I_L X_{eq2})^2}$$

PER UNIT

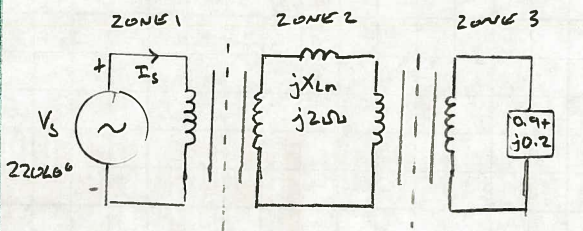

CHOOSE $\tilde{S}_b = 30 \text{ kVA}$ AND $V_{b2} = 480 \text{ V}$ IN ZONE 2

$$V_{b1} = V_{b2} \frac{240}{480} = 240 \text{ V} \quad V_{b3} = V_{b2} \frac{115}{460} = 120 \text{ V}$$

$$Z_{b1} = \frac{V_{b1}^2}{\tilde{S}_b} = \frac{240^2}{30000} = 1.92 \Omega \quad Z_{b3} = \frac{V_{b3}^2}{\tilde{S}_b} = 0.48 \Omega$$

$$Z_{b2} = \frac{V_{b2}^2}{\tilde{S}_b} = 7.68 \Omega$$

30 kVA 20 kVA

240/480V 460/115V


$Z_{eq1} = j0.768 \Omega$ $Z_{eq2} = j1.058 \Omega$

$$\dot{Z}_{T1} = \frac{Z_{eq1}(T1)}{Z_{b2}} = \frac{j0.768}{7.68} = j0.1 \text{ pu}$$

$$\dot{Z}_{L_n} = \frac{Z_{L_n}}{Z_{b2}} = \frac{j2}{7.68} = j0.2604 \text{ pu}$$

$$\dot{Z}_{T2} = \frac{Z_{eq}(T2)}{Z_{b2}} = \frac{j1.058}{7.68} = j0.1378 \text{ pu}$$
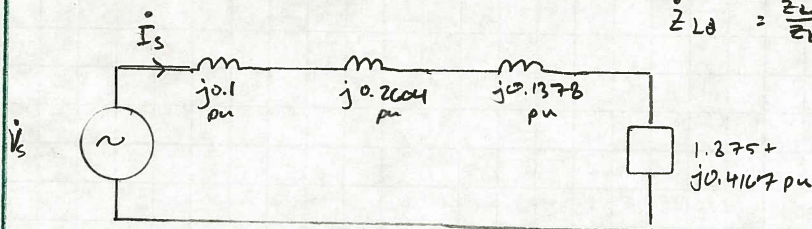
$$\dot{Z}_{L_0} = \frac{Z_{L_0}}{Z_{b3}} = \frac{0.9 + j0.2}{0.48} = 1.875 + j0.4167 \text{ pu}$$




$$\dot{V}_s = \frac{V_s}{V_{b1}} = \frac{220 \angle -20^\circ}{240} = 0.9167 \angle -20^\circ \text{ pu} \quad \dot{I}_s = \frac{\dot{V}_s}{\sum \dot{Z}} = 0.4395 \angle -26.01^\circ \text{ pu}$$

$$I_{b1} = \left(\frac{S_b}{V_{b1}}\right)^* = \frac{30000}{240} = 125 \text{ A} \quad I_{b2} = \left(\frac{S_b}{V_{b2}}\right)^* = \frac{30000}{480} = 62.5 \text{ A} \quad I_{b3} = \left(\frac{S_b}{V_{b3}}\right)^* = \frac{30000}{120} = 250 \text{ A}$$

$$I_L = \dot{I}_s I_{b3} = 109.88 \angle -26.01^\circ \text{ Arms} \quad I_{L_n} = \dot{I}_s I_{b2} = 27.45 \angle -26.01^\circ \text{ Arms}$$
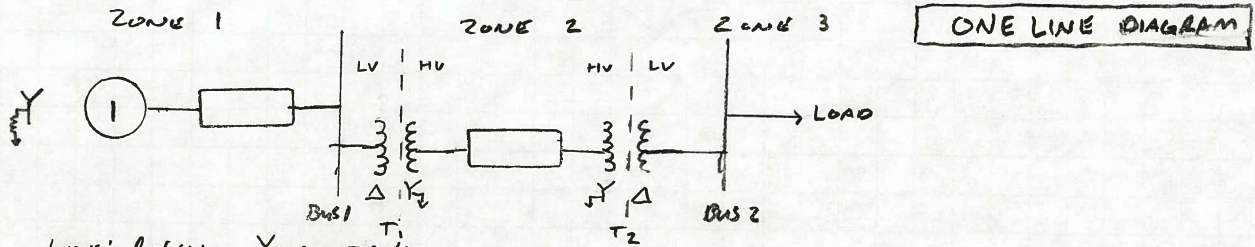
$$I_s = \dot{I}_s I_{b1} = 54.94 \angle -26.01^\circ \text{ Arms}$$



LINE: $l=64 \text{ km}$ $X_{Ln}=0.5 \Omega/\text{km}$
 GENERATOR: $\tilde{S}=300 \text{ MVA}$ $V=20 \text{ kV}$ $X_{GEN}=0.2 \text{ pu}$
 T_1 : $\tilde{S}=350 \text{ MVA}$ $230 \text{ kV Y}/20 \text{ kV } \Delta$ $X_{T1}=0.1 \text{ pu}$
 T_2 : $3 \times 1 \phi$. EACH $\tilde{S}_\phi=100 \text{ MVA}$ $127 \text{ kV Y}/13.2 \text{ kV } \Delta$ $X_{T2}=0.1 \text{ pu}$
 LOAD: $\tilde{S}=250 \text{ kVA @ pf: 0.8 LAGGING}$ $V=13.2 \text{ kV}$

1. CONVERT 1 ϕ UNITS TO 3 ϕ BANK

T_2 : $V_{AN} = \sqrt{3} V_{AB} = 220 \text{ kV}$ $\tilde{S}_T = 3 S_\phi = 300 \text{ MVA}$ $X'_{T2} = 0.1 \text{ pu}$
 T_2 : $\tilde{S}_T = 300 \text{ MVA}$ $220 \text{ kV}/13.2 \text{ kV}$ $X'_{T2} = 0.1 \text{ pu}$

2. DEFINE \tilde{S}_b FOR ENTIRE SYSTEM AND V_b FOR A ZONE.

LET $\tilde{S}_b = 500 \text{ MVA}$ AND LET $V_{b2,AB} = 230 \text{ kV} = V_{b0,HV}$ AND $20 \text{ kV} = V_{b0,LV}$

3. CALCULATE pu VALUES $V_{bi} = \frac{V_i}{V_0} \cdot V_{b0}$

$V_{b1} = V_{b0} \frac{V_1}{V_0} = 230 \text{ kV} \cdot \frac{20}{230} = 20 \text{ kV}$

$V_{b2} = V_{b0} \frac{V_2}{V_0} = 230 \text{ kV} \cdot \frac{13.2}{220} = 13.8 \text{ kV}$

CHANGE OF BASIS

GENERATOR': $X'_{GEN} = X_{GEN} \left(\frac{V_b}{V_0}\right)^2 \left(\frac{\tilde{S}_b'}{\tilde{S}_{GEN}}\right) = 0.2 \left(\frac{20 \text{ kV}}{20 \text{ kV}}\right)^2 \left(\frac{500 \text{ MVA}}{300 \text{ MVA}}\right) = 0.33 \text{ pu}$


T_1 : $X'_{T1} = X_{T1} \left(\frac{V_b}{V_0}\right)^2 \left(\frac{\tilde{S}_b'}{\tilde{S}_{GEN}}\right) = 0.1 \left(\frac{20 \text{ kV}}{20 \text{ kV}}\right)^2 \left(\frac{500 \text{ MVA}}{300 \text{ MVA}}\right) = 0.14286 \text{ pu}$

$Z_{b2} = \frac{V_{b0}^2}{\tilde{S}_b} = \frac{230^2}{500} = 105.8$ $X_{Ln} = 64 \text{ km} \frac{0.5 \Omega}{\text{km}} = 32 \Omega$ $X'_{Ln} = \frac{X_{Ln}}{Z_{b2}} = 0.302 \text{ pu}$

T_2 : $X'_{T2} = X_{T2} \left(\frac{V_b}{V_0}\right)^2 \left(\frac{\tilde{S}_b'}{\tilde{S}_{GEN}}\right) = 0.1 \left(\frac{230 \text{ kV}}{230 \text{ kV}}\right)^2 \left(\frac{500 \text{ MVA}}{300 \text{ MVA}}\right) = 0.1524 \text{ pu}$

4. DRAW EQUIVALENT PER-PHASE DIAGRAM

5. FIND ACTUAL VALUES

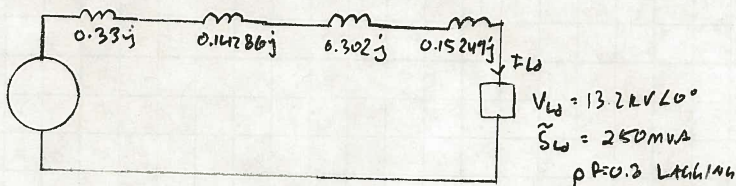


$\tilde{V}_{Ld} = \frac{V_{Ld}}{V_{b3}} = \frac{13.2 \text{ kV}}{13.8 \text{ kV}} = 0.9565 \angle 0^\circ \text{ pu}$

$\tilde{S}_{Ld} = \frac{\tilde{S}_{Ld}}{\tilde{S}_b} = \frac{250 \angle -36.87^\circ}{500} = 0.5 \angle -36.87^\circ \text{ pu}$


$\tilde{I}_{Ld} = \left(\frac{\tilde{S}_{Ld}}{\tilde{V}_{Ld}}\right)^* = 0.5227 \angle -36.87^\circ \text{ pu}$

\tilde{V} AT GEN. TERMINALS = $\tilde{V}_{Ld} + \tilde{I}_{Ld} (X'_{T2} + X'_{Ln} + X'_{T1}) = 1.171 \angle 12.327^\circ \text{ pu}$ $V_{GEN} = \tilde{V}_{GEN} \cdot V_{b1} = 23.42 \angle 12.327^\circ \text{ kV}_{rms}$

6. ADD PHASE SHIFT IF NEEDED.

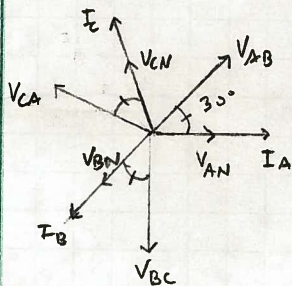

HV Y

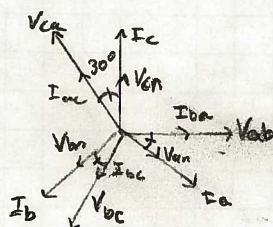


LV Δ

HV: $V_{AB} = V_{AN} \sqrt{3} \angle 30^\circ$

V_{AB} HV LEADS V_{ab} LV BY 30°

$\tilde{I}_{Ln} = \tilde{I}_{Ld} \cdot I_{b2} = 0.5227 \angle -36.87^\circ \cdot \frac{\tilde{S}_b}{\sqrt{3} V_{b2}} = 656 \angle -36.87^\circ = 656 \angle -4.87^\circ \text{ A}$

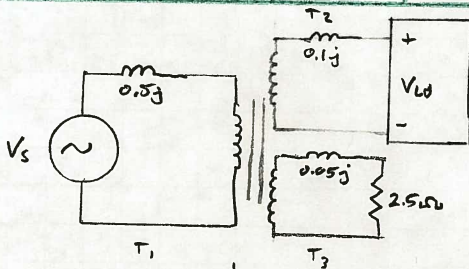$\tilde{I}_{Ld} = \tilde{I}_{Ld} \cdot I_{b3} = 0.5227 \angle -36.87^\circ \cdot \frac{\tilde{S}_b}{\sqrt{3} V_{b3}} = 10934.72 \angle -36.87^\circ \text{ A}$



$T_1: \tilde{S} = 100 \text{ kVA} \quad V = 1000 \text{ V}$


$T_2: \tilde{S} = 50 \text{ kVA} \quad V = 500 \text{ V}$

$T_3: \tilde{S} = 50 \text{ kVA} \quad V = 250 \text{ V}$

Load: $\tilde{S} = 50 \text{ kVA} @ \text{pf} = 1.0 \quad \bar{V}_{rated} = 500 \text{ V}$

$\frac{E_1}{N_1} = \frac{E_2}{N_2} = \frac{E_3}{N_3}$

STAR EQUIVALENT CIRCUIT

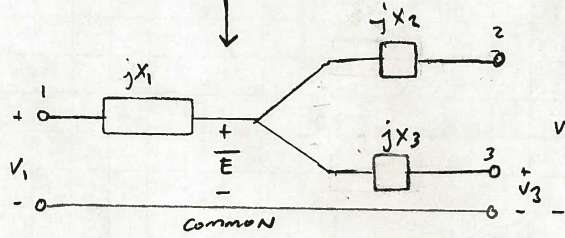

CHOOSE $\tilde{S}_b = 100 \text{ kVA}$ AND $V_{b1} = 1000 \text{ V} = V_{b0}$

$V_{b2} = V_{b0} \cdot \frac{V_2}{V_1} = 500 \text{ V} \quad V_{b3} = V_{b0} \cdot \frac{V_3}{V_1} = 250 \text{ V}$

$Z_{b1} = \frac{V_{b1}^2}{S_b} = 10 \Omega \quad Z_{b2} = \frac{V_{b2}^2}{S_b} = 2.5 \Omega \quad Z_{b3} = \frac{V_{b3}^2}{S_b} = 0.625 \Omega$

$Z_{b2+} = \frac{V_{b3}^2}{S_b} = 0.625 \Omega$

$\dot{Z}_1 = \frac{Z_1}{Z_{b1}} = 0.05j \text{ pu} \quad \dot{Z}_2 = \frac{Z_2}{Z_{b2}} = 0.04j \text{ pu} \quad \dot{Z}_3 = \frac{Z_3}{Z_{b3}} = 0.08j \text{ pu} \quad \dot{Z}_{2.5} = \frac{Z_{2.5}}{Z_{b3}} = 4 \text{ pu}$

$\dot{V}_{Ld} = \frac{V_{Ld}}{V_{b2}} = 1 \angle 0^\circ \text{ pu} \quad \dot{I}_{Ld} = \left(\frac{\dot{S}_{Ld}}{\dot{V}_{Ld}} \right)^* = 0.5 \angle 0^\circ \text{ pu}$


$\dot{E} = \dot{V}_{Ld} + \dot{I}_{Ld} + jX_2 = 1 + 0.02j \text{ pu}$

$\dot{I}_3 = \frac{\dot{E}}{jX_3 + Z_3} = 0.25 \angle 0^\circ \text{ pu}$

$\dot{I}_1 = \dot{I}_2 + \dot{I}_3 = 0.75 \angle 0^\circ \text{ pu}$

$\dot{V}_1 = \dot{E} + \dot{I}_1 jX_1 = 1.00165 \angle 3.29^\circ \text{ pu}$

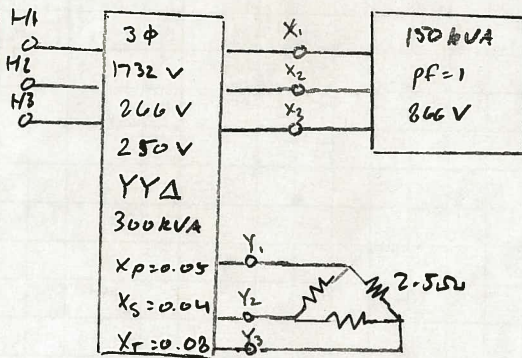
$\dot{V}_s = \dot{V}_1 V_{b1} = 1001.65 \angle 3.29^\circ \text{ V rms}$



CHOOSE $\tilde{S}_b = 300 \text{ kVA}$

$V_{b1,AB} = 1732 \text{ V} \quad V_{b2,AC} = 866 \text{ V} \quad V_{b3,BC} = 250 \text{ V}$




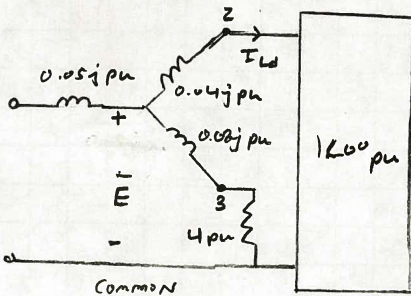
$Z_Y = \frac{Z_\Delta}{3} = \frac{2.5}{3} \quad \dot{Z}_Y = \frac{Z_Y}{Z_b} = \frac{Z_Y}{\frac{V_{b3,AC}^2}{S_b}} = 4 \text{ pu}$







$\dot{I}_{Ld} = \frac{\dot{S}_{Ld}}{\dot{V}_{Ld}} = 0.5 \angle 0^\circ$

$\dot{E} = \dot{V}_{Ld} + \dot{I}_{Ld} \cdot jX_2 = 1.0002 \angle 1.146^\circ \text{ pu}$

AMPAD

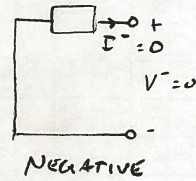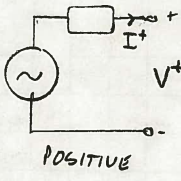
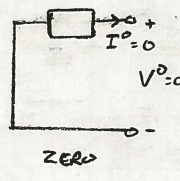
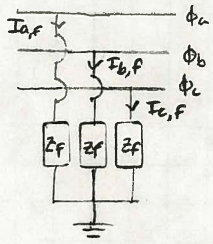


3Φ FAULT

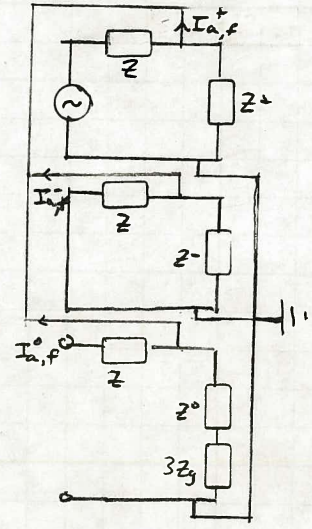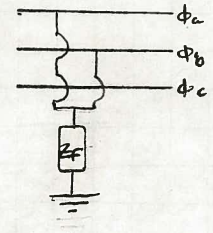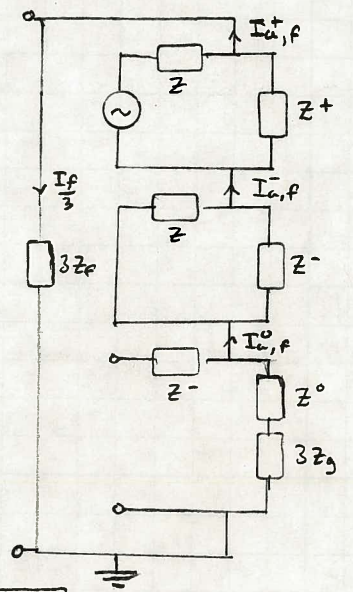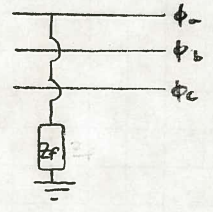


SLG FAULT

DLL FAULT

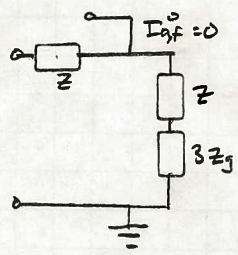
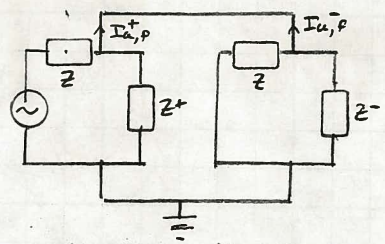
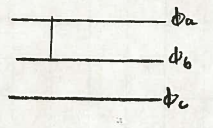


L-L FAULT

ONE LINE DIAGRAM EXAMPLE

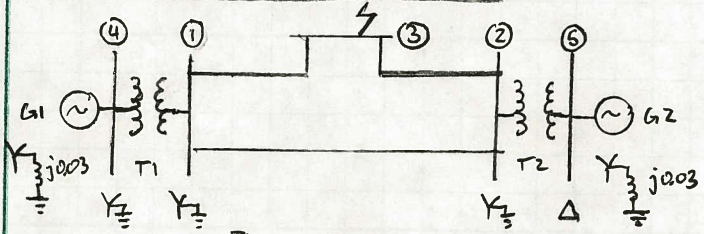


Item	MVA	kV	X ⁺	X ⁻	X ⁰
G1	100	25	0.2	0.2	0.05
G2	100	13.8	0.2	0.2	0.05
T1	100	25/230	0.05	0.05	0.05
T2	100	13.8/230	0.05	0.05	0.05
TL12	100	230	0.1	0.1	0.3
TL13	100	230	0.1	0.1	0.3
TL23	100	230	0.1	0.1	0.3

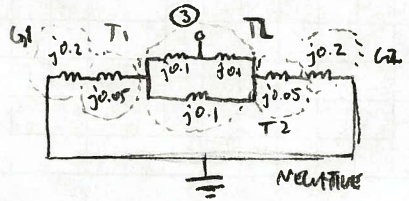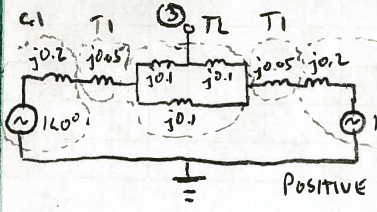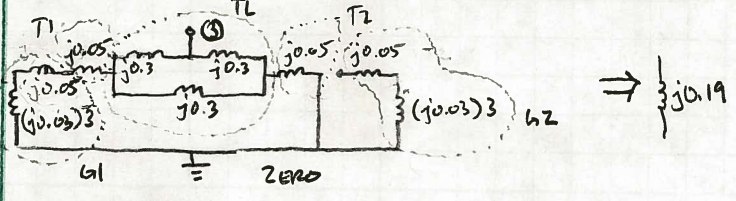

⇒ j0.175

POWER FLOW ANALYSIS

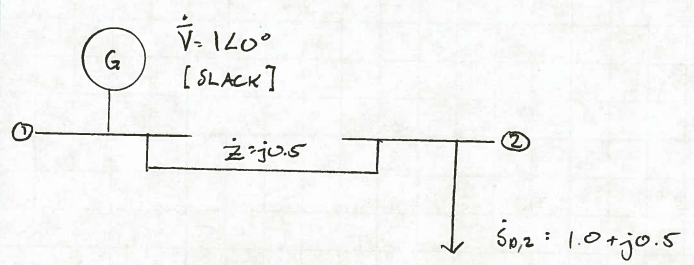

Find $|V_2^{(1)}|$, $\phi_2^{(1)}$, $\tilde{P}_{12}^{(1)}$

$Y_{Ln} = (Z_{Ln})^{-1} = -j2$ $Y_{Bus} = j \begin{bmatrix} -2 & 2 \\ 2 & -2 \end{bmatrix}$

GAUSS-SEIDEL: $V_i^{(k+1)} = \frac{1}{Y_{ii}} \left[\left(\frac{S_i}{V_i^{(k)}} \right)^* - \sum_{j \neq i} Y_{ij} V_j^{(k)} \right]$

Assume FLAT PROFILE: $|V_2^{(0)}| = 1$, $\phi_2^{(0)} = 0^\circ$ $Y_{11} = Y_{22} = -j2$ $S_i = S_{D,2} = -(1.0 + j0.5)$
 $\tilde{V}_2^{(1)} = \frac{1}{-j2} \left[\left(\frac{-1.0 - j0.5}{1.0 \angle 0^\circ} \right)^* - j2(1.0 \angle 0^\circ) \right] = 0.901 \angle -33.7^\circ$
 $\tilde{P}_{12} = V_1 (Y_{11}^* V_1 + Y_{12}^* V_2^*) = 1.12 \angle 26.57^\circ$

NEWTON-RAPHSON $\tilde{P}_2 = |V_2| \sum_{j \neq 2} |V_j| j B_{2j} \sin \phi_{2j}$ $\tilde{Q}_2 = |V_2| \sum_{j \neq 2} |V_j| -j B_{2j} \cos \phi_{2j} - |V_2|^2 B_{22}$
 $B = \begin{bmatrix} -2 & 2 \\ 2 & -2 \end{bmatrix}$ $\tilde{x} = \begin{bmatrix} \phi_2 \\ |V_2| \end{bmatrix}$ $f(\tilde{x}) = \begin{bmatrix} P_2(\tilde{x}) \\ Q_2(\tilde{x}) \end{bmatrix}$ FLAT PROFILE: $\tilde{x}^{(0)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$


$\tilde{P}_2(\tilde{x}) = |V_2| |V_1| B_{21} \sin(\phi_2 - \phi_1) = 2|V_2| \sin \phi_2$ $\tilde{Q}_2(\tilde{x}) = -[|V_2| |V_1| B_{21} \cos(\phi_2 - \phi_1) + |V_2|^2 B_{22}]$
 $= -2|V_2| \cos \phi_2 + 2|V_2|^2$

$J(\tilde{x}) = \begin{bmatrix} \frac{\partial P_2}{\partial \phi_2} & \frac{\partial P_2}{\partial |V_2|} \\ \frac{\partial Q_2}{\partial \phi_2} & \frac{\partial Q_2}{\partial |V_2|} \end{bmatrix} = \begin{bmatrix} -2|V_2| \cos \phi_2 & 0 \\ 0 & -2|V_2| \cos \phi_2 + 2|V_2|^2 \end{bmatrix}$
 $J(\tilde{x}^{(0)}) = \begin{bmatrix} 2 & 0 \\ 0 & 2 \end{bmatrix}$ $f(\tilde{x}^{(0)}) = \begin{bmatrix} -1.0 \\ -0.5 \end{bmatrix}$ $\tilde{x}^{(k+1)} = \tilde{x}^{(k)} - J(\tilde{x}^{(k)})^{-1} f(\tilde{x}^{(k)})$
 $\tilde{x}^{(1)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} - \begin{bmatrix} 2 & 0 \\ 0 & 2 \end{bmatrix}^{-1} \begin{bmatrix} -1.0 \\ -0.5 \end{bmatrix} = \begin{bmatrix} -28.65^\circ \\ 0.75 \end{bmatrix} = \begin{bmatrix} \phi_2^{(1)} \\ |V_2^{(1)}| \end{bmatrix}$ $\tilde{P}_{12}^{(1)} = 0.99 \angle 43.55^\circ$

FAST DECOUPLE

$J(\tilde{x}) = \begin{bmatrix} J1(\tilde{x}) & 0 \\ 0 & J2(\tilde{x}) \end{bmatrix}$ $J1(\tilde{x}) = \begin{bmatrix} -2 & 0 \\ 0 & -2 \end{bmatrix}$
 $\phi^{(k+1)} = \phi^{(k)} - J1(\tilde{x}^{(k)})^{-1} \frac{\Delta \tilde{P}^{(k)}}{|V|}$ $|V|^{(k+1)} = |V|^{(k)} - J2(\tilde{x}^{(k)})^{-1} \frac{\Delta \tilde{Q}^{(k)}}{|V|}$
 $\Delta \tilde{P}^{(0)} = [-1]$ $\phi^{(0)} = [0]$ $|V|^{(0)} = [1]$ $\Delta \tilde{Q}^{(0)} = [-0.5]$
 $\phi^{(1)} = -28.65^\circ$ $|V|^{(1)} = 0.75$
 $\tilde{P}_{12} = 0.99 \angle 43.55^\circ$


FAULT ANALYSIS

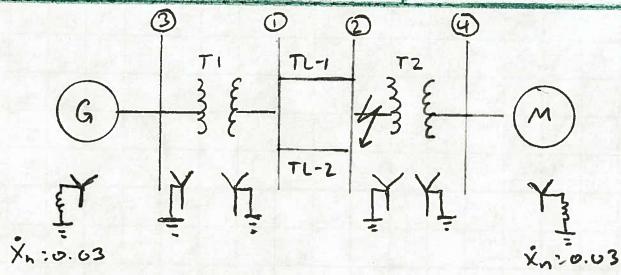

	MVA	KV	X ⁺	X ⁻	X ⁰
G	100	25	0.2	0.2	0.05
M	100	13.8	0.2	0.2	0.05
T1	100	25/230	0.05	0.05	0.05
T2	100	13.8/230	0.05	0.05	0.05
TL-1	100	230	0.1	0.1	0.3
TL-2	100	230	0.2	0.2	0.3


$\bar{V}_F = 1.05 \angle 0^\circ$

POSITIVE SEQUENCE

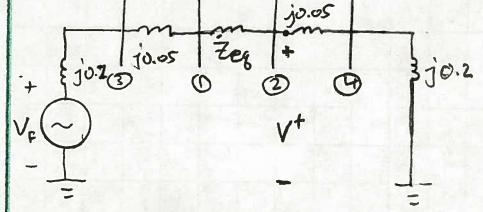


$$\bar{Z}_{eq} = j0.1 \parallel j0.2 = j0.067$$

THEVENIN EQUIVALENT

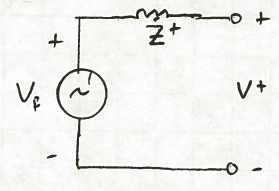


$$\bar{Z}^+ = (j0.067 + j0.25) \parallel j0.25 = j0.1397$$

NEGATIVE SEQUENCE

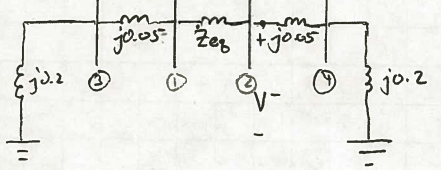


$$\bar{Z}_{eq} = j0.1 \parallel j0.2 = j0.067$$

-THEVENIN EQUIVALENT

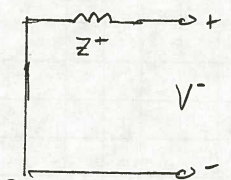


$$\bar{Z}^- = (j0.067 + j0.25) \parallel j0.25 = j0.1397$$

ZERO SEQUENCE

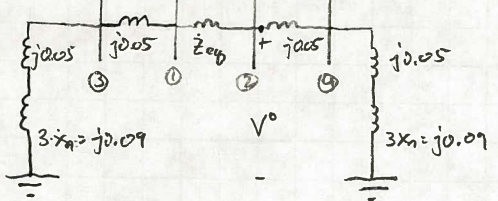

$$\bar{Z}_{eq} = j0.3 \parallel j0.3 = j0.15$$

THEVENIN EQUIVALENT

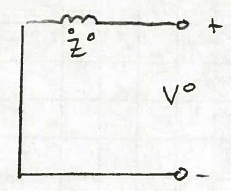

$$\bar{Z}^0 = (j0.09 + j0.05 + j0.05 + j0.15) \parallel (j0.05 + j0.05 + j0.09) = j0.122$$

3Φ SC BALANCED

$V^0 = V^- = 0 \quad I^0 = I^- = 0$

$\bar{I}^+ = \frac{\bar{V}_F}{\bar{Z}^+} = \frac{1.05 \angle 0^\circ}{j0.1397} = 7.52 \angle -90^\circ$

$\bar{I}^{0+} = \langle 0, 7.52 \angle -90^\circ, 0 \rangle$

$\bar{I}_{abc}^f = A \cdot \bar{I}^{0+} = \langle 7.52 \angle 40^\circ, 7.52 \angle 150^\circ, 7.52 \angle 300^\circ \rangle$

SLG

$\bar{I}^0 = I^- = \bar{I}^+ = \frac{\bar{V}^+}{\bar{Z}^+ + \bar{Z}^- + \bar{Z}^0} = \frac{1.05 \angle 0^\circ}{j0.4013} = 2.617 \angle -90^\circ$

$\bar{I}^{0+} = \langle 2.617 \angle -90^\circ, 2.617 \angle -90^\circ, 2.617 \angle -90^\circ \rangle$

$\bar{I}_{abc}^f = A \cdot \bar{I}^{0+} = \langle 7.85 \angle -90^\circ, 0, 0 \rangle$

LL

$I^0 = 0 \quad I^+ = -I^- = \frac{V^+}{\bar{Z}^+ + \bar{Z}^-} = \frac{1.05 \angle 0^\circ}{j0.2794} = 3.758 \angle -90^\circ$

$\bar{I}^{0+} = \langle 0, 3.758 \angle -90^\circ, 3.758 \angle -90^\circ \rangle$

$\bar{I}_{abc}^f = \langle 0, -6.5, 6.5 \rangle$

DLG

$\bar{I}^+ = \frac{V^+}{\bar{Z}^+ + 2\bar{Z}^-} = \frac{1.05 \angle 0^\circ}{j0.205} = 5.127 \angle 90^\circ$


$\bar{I}^- = -\bar{I}^+ \left(\frac{\bar{Z}^0}{2\bar{Z}^-} \right) = -5.127 \angle -90^\circ (0.466) = 2.389 \angle 90^\circ$

$\bar{I}^0 = -(\bar{I}^+ + \bar{I}^-) = 2.738 \angle -90^\circ$

$\bar{I}^{0+} = \langle 2.738 \angle -90^\circ, 5.127 \angle 90^\circ, 2.389 \angle 90^\circ \rangle$

$\bar{I}_{abc}^f = \langle 0, 7.696 \angle 147.75^\circ, 7.696 \angle 32.25^\circ \rangle$

CURRENT TRANSFORMER

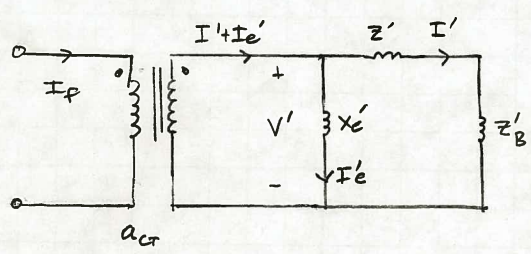


I' = SECONDARY OUTPUT
 Z' = SECONDARY LEAK IMPEDANCE
 Z_B = IMPEDANCE OF TERM. DEVICES

1. $a_{CT} \rightarrow Z'$ (FIG. 10.8)
2. Assume I', Z_B
3. $V' = (Z' + Z_B) I'$
4. $(V', a_{CT}) \rightarrow I_e'$ (FIG 10.8)
5. $I_f = a_{CT} (I' + I_e')$
6. $e = \frac{I_e'}{I' + I_e'}$

$$(I' + I_e') = \frac{I_{RATED}}{a} \approx I'$$

OVERCURRENT RELAY PROTECTION

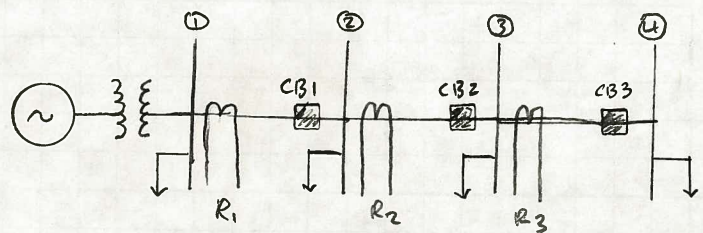

$$\frac{I_f}{a_{CT}} = \frac{(I' + I_e')_f}{(I' + I_e')_f}$$

$$M = \frac{(I' + I_e')_f}{I}$$

$$t_{clear} = t_{trip} + t_{cyc}$$

$$t_{cyc} = \frac{N_{cyc}}{60}$$

$$t = TD \left(0.0963 + \frac{3.88}{M^2 - 1} \right)$$

$R_1: a_{CT} = 800:5 \quad I_R = 700A \quad R_2: a_{CT} = 600:5 \quad I_R = 350A \quad R_3: a_{CT} = 600:5 \quad I_R = 250A$

EACH CB HAS $N_{cyc} = 5 \rightarrow t_{cyc} = \frac{5}{60} s = 0.083 s$
 $t_{COORD} = 0.3 s$

$$CT_3: \frac{(I' + I_e')_f}{a_{CT}} = \frac{I_R}{600/5} = \frac{250}{600/5} = 2.08 \approx I' \Rightarrow T_3 = 2.5$$


$$CT_1: \frac{I_A}{a_{CT}} = \frac{700}{800/5} = 4.38 \Rightarrow T_1 = 5$$

$$CT_2: \frac{I_R}{a_{CT}} = \frac{350}{600/5} = 2.91 \Rightarrow T_2 = 3$$

FAULT SCENARIO: FAULT IN 3-4, $I_f = 2600A, TD_3 = 0.5$
 $(I' + I_e')_f = \frac{2600A}{600/5} = 21.67A \quad M_3 = \frac{(I' + I_e')_f}{I_3} = \frac{21.67}{2.5} = 8.67$
 $(M_3 = 8.67, TD_3 = 0.5) \rightarrow t_{trip} = 0.1 s \quad (FIG 10.12)$
 $t_{clear} = t_{trip} + t_{cyc} = 0.1 s + 0.083 s = 0.183 s$

FAULT SCENARIO: FAULT IN 3-4, $I_f = 2600A, TD_3 = 0.5, CB_3$ MALFUNCTIONS
 $t_{trip} = t_{clear} + t_{COORD} = 0.183 s + 0.3 s = 0.483 s$
 $(I' + I_e')_f = \frac{I_f}{a_{CT}} = \frac{2600A}{600/5} = 21.67A$
 $M_2 = \frac{(I' + I_e')_f}{I_2} = \frac{21.67}{3} = 7.22$
 $(M_2 = 7.22, t_{trip} = 0.483 s) \rightarrow TD_2 = 2 \quad (FIG 10.12)$

AMPAD

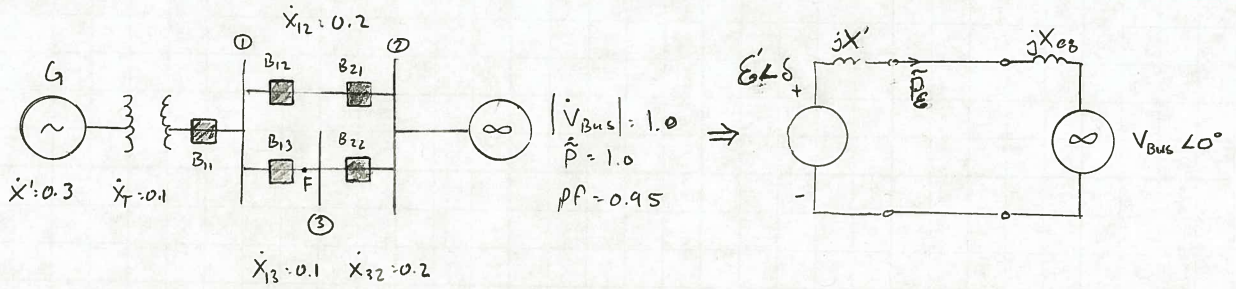

PRE-FAULT:

$$X_{eq} = (0.3 + 0.1 + 0.2) \parallel (0.1 + 0.2) = 0.52$$

$$I = \frac{P_{Fault}}{V_{Bus} \cdot PF} \angle -\cos^{-1}(PF) = \frac{1.0}{1.0 \cdot 0.95} \angle -\cos^{-1}(0.95) = 1.053 \angle -18.2^\circ \text{ pu}$$


$$E' = V_{Bus} + jX_{eq}I = 1.0 \angle 0^\circ + j0.52(1.053 \angle -18.2^\circ) = 1.28 \angle 23.9^\circ \text{ pu}$$

$$\tilde{P}_E = \frac{E' V_{Bus}}{X_{eq}} \sin \delta = \frac{1.28(1.0)}{0.52} \sin \delta = 2.46 \sin \delta \text{ pu}$$

FAULT SCENARIO: B_{12} INADVERTENTLY OPENS

$$X_{eq} = 0.3 + 0.1 + 0.1 + 0.2 = 0.7$$
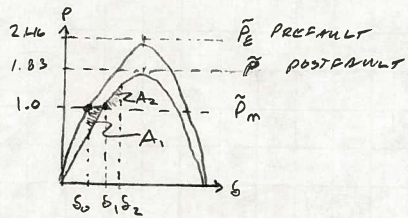
$$\tilde{P}_E = \frac{1.28(1.0)}{0.7} \sin \delta = 1.83 \sin \delta$$



$$A_2 = A_1$$

$$2.46 \sin \delta_0 = 1 \rightarrow \delta_0 = 23.95^\circ$$


$$1.83 \sin \delta_1 = 1 \rightarrow \delta_1 = 33.12^\circ$$

$$\int_{23.95^\circ}^{33.12^\circ} (2.46 \sin \delta - 1) d\delta = \int_{33.12^\circ}^{\delta_2} (1.83 \sin \delta - 1) d\delta \rightarrow \delta_2 = 42.63^\circ$$

FAULT SCENARIO: 3 ϕ TO GROUND FAULT AT F, B_{13} AND B_{12} OPEN

$$X_{eq} = 0.3 + 0.1 + 0.2 = 0.6$$
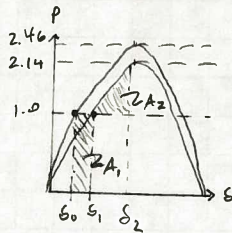
$$\tilde{P}_E = \frac{1.28(1.0)}{0.6} \sin \delta = 2.14 \sin \delta$$



$$2.46 \sin \delta_0 = 1 \rightarrow \delta_0 = 23.95^\circ$$



$$2.14 \sin \delta_1 = 1 \rightarrow \delta_1 = 27.90^\circ$$

$$\int_{23.95^\circ}^{27.90^\circ} (2.46 \sin \delta - 1) d\delta = \int_{27.90^\circ}^{\delta_2} (2.14 \sin \delta - 1) d\delta \rightarrow \delta_2 = 43.23^\circ$$

AMPAD

AMPAD



LOW PASS

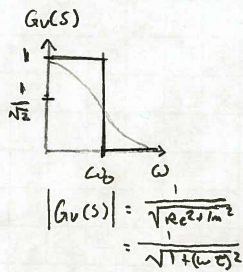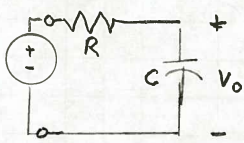

$$G_v(s) = \frac{1}{1+j\omega\tau} \quad \tau = RC$$

$$\phi(\omega) = \tan^{-1}(\omega\tau)$$

HIGH PASS

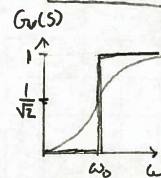
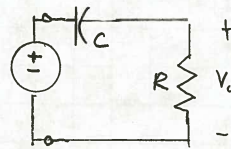


$$G_v(s) = \frac{j\omega\tau}{1+j\omega\tau} \quad \tau = RC$$



$$\phi(\omega) = \frac{\pi}{2} - \tan^{-1}(\omega\tau)$$

VARIABLE FREQ. RESPONSE

BAND PASS

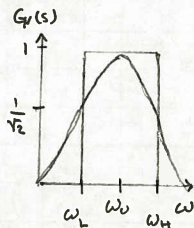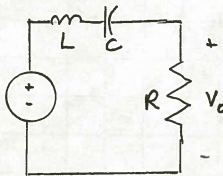

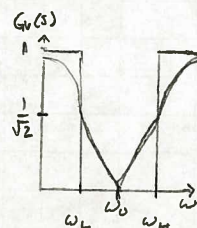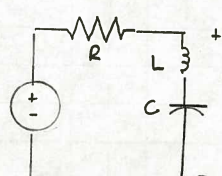
$$G_v(s) = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$




$\beta \quad f_Q \uparrow \Rightarrow \beta \downarrow$


RESONANCE

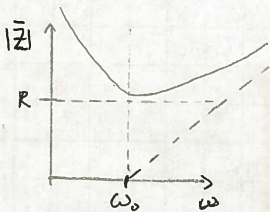

SERIES

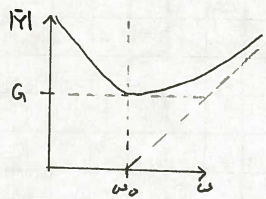


PARALLEL

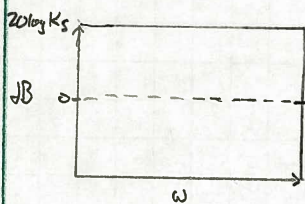


$$H(j\omega) = K_s$$

FREQ. INDEPENDENT

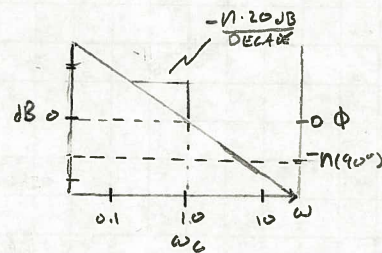


$$H(j\omega) = \frac{1}{(\tau j\omega)^n} \quad \omega_c = \frac{1}{\tau}$$

POLE AT ORIGIN

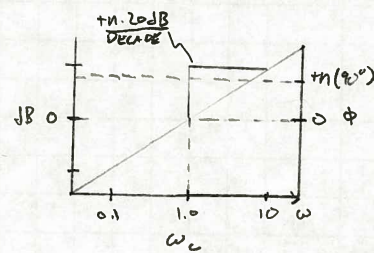

$$H(j\omega) = \frac{(\tau j\omega)^n}{1}$$


ZERO AT ORIGIN

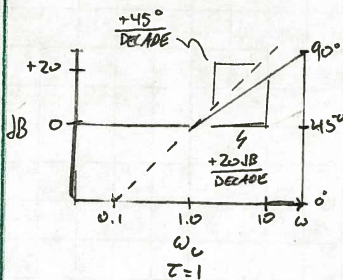

$$|B| = 20 \log_{10} |1+j\omega\tau|$$

$$\phi = \tan^{-1}(\omega\tau)$$

SIMPLE ZERO

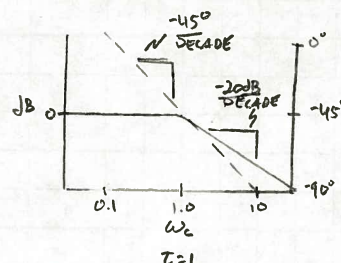

$$|B| = 20 \log_{10} |(1+j\omega\tau)^{-1}|$$

$$\phi = \tan^{-1}(\omega\tau)$$

SIMPLE POLE